

# Lecture 16 In-Class Worksheet



## 1 Learning Objectives

This worksheet is based on Lumetta course notes section 2.5 and Patt & Patel textbook section 3.3. After completing this lesson, you will know how to:


- [S16-1] Build a decoder with a set of arbitrary parameters.
- [S16-2] Build a multiplexer with a set of arbitrary parameters.
- [S16-3] Implement arbitrary functions using a decoder and **OR** gate.
- [S16-4] Implement arbitrary functions using a multiplexer.
  
## 2 Decoders


A *decoder* is a logic device that takes  $n$  bits of input and produces  $2^n$  bits out output. The general form of a decoder is shown on the right. Exactly one of the output bits of the decoder is 1 and the others are all 0. Which bit is 1 is determined by the input: each input corresponds to a distinct output bit being one. A common scheme is to treat the  $n$  bits of input as a binary number that encodes which of the  $2^n$  output bits is 1. For example, shown below on the left is a 2-to-4 decoder and its truth table. The diagram on the right shows its implementation using **AND** gates.




$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

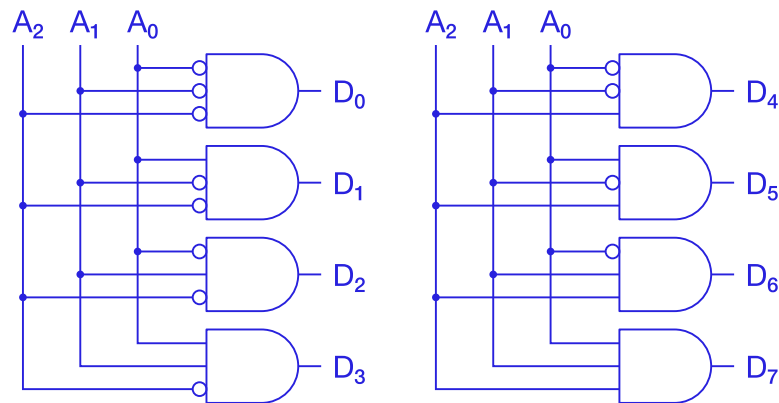**Q1.** Implement a 3-to-8 decoder using AND gates and inverters.



**The outputs of a  $n$ -to- $2^n$  decoder are all of the minterms of a function on  $n$  variables.** Recall that to construct the canonical SOP expression for a Boolean function, we OR-ed all of its minterm implicants (minterms corresponding to inputs where the function had value 1). We can thus implement an arbitrary function by OR-ing the appropriate subset of the outputs of a decoder. For example, to implement the XOR function on two variables, we can use a 2-to-4 decoder to produce the minterms on  $A$  and  $B$ , and then OR the appropriate minterms:

 


**Q2.** Implement the following function using a 3-to-8 decoder and an OR gate:

$$M(S, A, B) = \begin{cases} A & \text{if } S = 0, \\ B & \text{if } S = 1. \end{cases}$$

The truth table for  $M$  is shown on the left and final circuit on the right.


$S$	$A$	$B$	$M$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

 
### 3 Multiplexers

A  $2^n$ -to-1 multiplexer is a logic device that takes an  $n$ -bit *select* input (also called *selector*) and  $2^n$  data inputs, and produces a single bit of output. The select input determines which of the  $2^n$  possible inputs are sent to the output. In general, each of the  $2^n$  inputs may be  $m$ -bits wide, in which case the multiplexer output is also  $m$  bits wide, giving a  $m2^n$ -to- $m$  multiplexer. Such a multiplexer is equivalent to  $m$   $2^n$ -to-1 multiplexers with a common select input.

The diagram symbol, function summary, and implementation of a 4-to-1 multiplexer is shown below. The trapezoidal symbol shown below is the standard symbol for a multiplexer.




$S_1$	$S_0$	$D$
0	0	$A_0$
0	1	$A_1$
1	0	$A_2$
1	1	$A_3$

 

**Q3.** Implement a two-input XOR function using a 4-to-1 multiplexer.

## Lecture 16 In-Class Worksheet

 

**Q4.** Implement a two-input XOR function using a 2-to-1 multiplexer and inverters.

