

# Lecture 18 In-Class Worksheet


## 1 Learning Objectives

This worksheet is based on Lumetta course notes section 2.7. After completing this lesson, you will know how to:

- [S18-1] Construct a register that supports any combination of: load enable, parallel load, serial load, and bit shifts.

 
## 2 Registers

A *register* is a set of one or more flip-flops with a common clock. The simplest kind of register is just a set of  $n$  flip-flops with a common clock. A 4-bit register of this type is shown below. This register supports *parallel load*, meaning that all 4 bits can be loaded in one cycle.



 
## 3 Load Control

The simple register above loads a new set of bits on every clock cycle. We can add a control signal to allow us to keep the value currently stored in the register ( $LD = 0$ ) or update it using the provided input ( $LD = 1$ ) on the rising edge of the clock. A 3-bit register of this type is shown below.



 
## 4 Shift Registers

A *shift register* receives its input 1 bit at a time, shifting bits internally on each cycle. A 4-bit register of this type is shown below. On each rising edge of the clock, all values are shifted one bit to the right and *SI* is shifted into the left-most register bit.



 We can also add a control signal to allow us to keep the value currently stored in the register ( $SH = 0$ ) or to shift the values one bit to the right ( $SH = 1$ ).




## 5 Registers with Combinations of Features

We can combine the mechanisms above to create any combination of features, such as the registers shown in the Lumetta course notes, section 2.7.


**Q1.** Create a register with parallel inputs and outputs and a control signal  $LD/\overline{RR}$  where  $LD/\overline{RR} = 1$  causes the register to be loaded in parallel and  $LD/\overline{RR} = 0$  causes the bits to rotate right. (In a *rotate* operation, the bit shifted out one side is shifted in at the other. For example, rotating the 4-bit value 1011 right one bit gives 1101.)

## Lecture 18 In-Class Worksheet

 
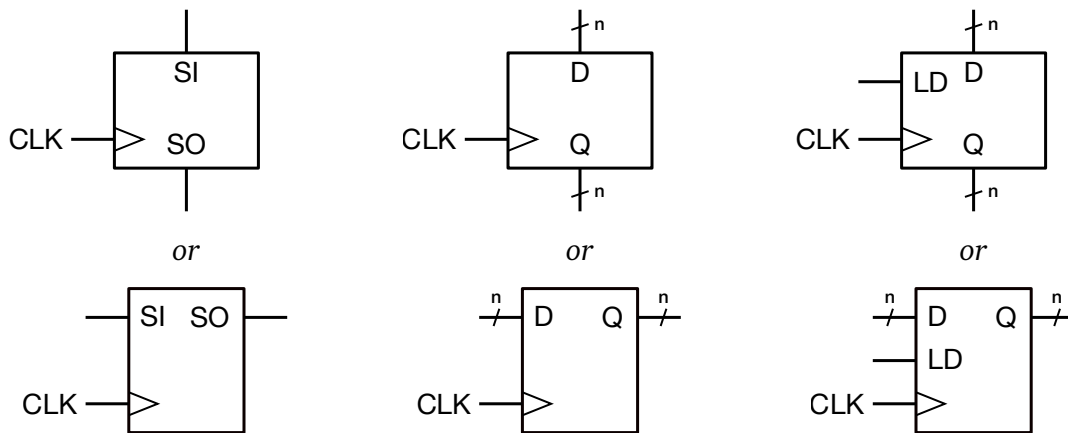
## 6 Diagram Symbols

As with other devices we have built so far, we represent a register using a box with inputs and outputs, hiding its exact implementation. It is usually possible to tell what a register does from the names of the input and output signals it has. Shown below are several such symbols.




**Q2.** Match the symbols shown above to the registers described in Sections 2–4.

## 7 Building Counters Using Registers


We will use registers extensively throughout the remainder of the class to build complex devices. However, we can already build some useful devices combining a register with some additional logic.

Shown on the right is a  $n$ -bit *counter*, a device that counts the number of clock cycles. The device labeled INCR is an incrementer: it adds one to the input. As discussed in Question 3 on Worksheet 13, we can build an  $n$ -bit incrementer using an  $n$ -bit adder.

 Unfortunately, while the counter above does count, it is not very useful: we can't control its starting value or when it starts counting.



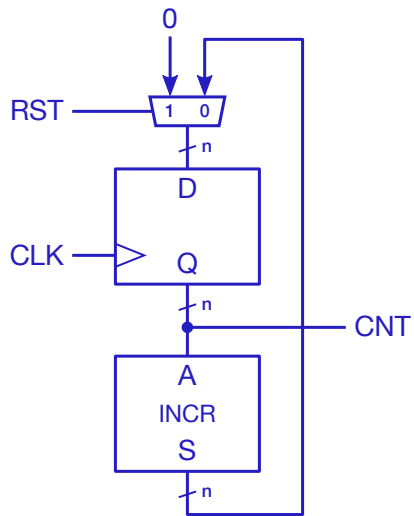**Q3.** Add a reset input signal to the counter above that resets the counter to zero. When  $RST = 1$ , the counter value should reset to zero on the next rising edge of the clock. When  $RST = 0$ , the counter value should increment on the rising edge of the clock.



**Q4.** Add a input signal to the counter in Q3 above that pauses the counter. When  $RUN = 1$ , the counter should count. When  $RUN = 0$ , the counter value should not change on the rising edge of the clock.

The figures below show two different possible implementations.

