

University of Illinois at Urbana-Champaign  
Dept. of Electrical and Computer Engineering

# ECE 120: Introduction to Computing

---

## Storing a Bit: the Gated D Latch

# Everything So Far Has Been Combinational Logic

---

So far, we have talked only about **combinational logic**.

Combinational logic allows us to solve the following type of problem:

- given a set of bits as input,
- how can we combine them to produce other sets of bits (Boolean expressions)?

**But where do the input bits come from?**

# Now Let's Look at Sequential Logic

---

Today, we will start to look at **sequential logic**.

Sequential logic

- **stores bits as state**, and
- its **behavior depends on the state** (the values of the stored bits),
- just like the behavior of a C program can depend on the current values of variables.

# A Dual “Inverter” Loop Serves a Specific Purpose

---

What is a 1-input NAND gate?


An inverter / NOT.

Remember the gate structures?

What does the circuit here do?

It has no inputs!

How can we analyze it?

 

# Start Solving by Picking a Value for Some Variable

First, **write a truth table.**

Then **pick a value.**


Say  **$Q = 0$ .**

**Which implies what about P?**

**$P = 1$ .**

**Which implies what about Q?**


**$Q = 0$  (be sure to check!).**

 

Q	P
0	1
 
# Trace Logic Values to Find Stable States

We say that this state ( $Q = 0$ , and  $P = 1$ , as shown in the truth table) is **stable** because the values do not continue to change forever.



What if we instead pick  $Q = 1$ ?

**In that case, what is P?**


**And what does  $P = 0$  imply for Q?**

**Again, be sure to check stability.**

Q	P
0	1
1	0
 
# The Dual-Inverter Loop Stores One Bit

We say that this circuit is **bistable** because it has **two stable states** (bi- = two).



Bits on a chip are typically stored using this kind of dual-inverter loop.

But ... **how do we set a value?**

Q	P
0	1
1	0

# Use an Extra Input to Set the Bit Q

Let's add an input.

We will call it **S'**.


**What happens when S' is 1?**

The new input has no effect!  
(green is the previous truth table)

**What if S' = 0?**

**Q = 1!** And **P = 0**.

So **S'** Sets the bit **Q** to 1.

 

S'	Q	P
0	1	0
1	0	1
1	1	0



# Active Low Inputs are Named with “Bar” (NOT)

---

Why did we call the input **S'**?

(Call it “S bar,” by the way.)

The action induced by **S'**,

- to **S(et) the bit Q**,
- occurs when **S' = 0** (S' is low).

We say that the input S' is **active low**.

And we name it **S'** instead of **S** to indicate how the input should be used.


# What About Resetting Q to 0?

So we can set  $Q = 1$ .

But ... what if we want  $Q = 0$ ?

Keep flipping the power on and off until we get lucky?  
(Maybe not.)

Any ideas?

 

$S'$	$Q$	$P$
0	1	0
1	1	0
1	0	1

# Use an Extra Input to Reset the Bit Q

Another input? Sure.

We will call it **R'**.


**What happens when R' is 1?**

The new input has no effect!  
(green is the previous table)

**What if R' = 0 and S' = 1?**

**P = 1!** And **Q = 0.**

So **R' Resets the bit Q to 0.**

 

R'	S'	Q	P
0	1	0	1
1	0	1	0
1	1	0	1
1	1	1	0


# An R'-S' Latch Consists of Two NAND Gates

This circuit has a name!

It's an **R'-S' latch**  
("R bar, S bar latch").

Store a **1 bit** by  
lowering **S'** to 0.

 Store a **0 bit** by  
lowering **R'** to 0'.



R'	S'	Q	P
0	1	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# Avoid Setting Both $S'$ and $R'$ to 0 Simultaneously


What if we set both  $S'$  and  $R'$  to 0 at the same time?

$Q = 1$  and  $P = 1$ .


But when we raise the inputs, we may leave the stored bit in either state.

Or, worse, the loop may not settle into digital voltages (**metastable**).

**Do NOT lower both at once!**

 
 
# Extra Gates Prevent the Forbidden Input Combination




We can add a couple more NAND gates to prevent setting both **S'** and **R'** to 0.

Let's check the truth table.

So **Q** stores **D**...

<b>D</b>	<b>R'</b>	<b>S'</b>	<b>Q</b>	<b>P</b>
<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>
 
# We Can Simplify the Design to Copy D to Q




**There's an easier way** to implement such a circuit, though...

So **Q** stores **D**...

D	R'	S'	Q	P
0	0	1	0	1
1	1	0	1	0

# Extra Inputs Control Copying of D to Q

 

Let's add more inputs to the new gates, too.

Now our design only copies **D** to **Q** when **WE = 1**.

WE	D	R'	S'	Q	P
1	0	0	1	0	1
1	1	1	0	1	0



# The Circuit Can Also Store a Bit


## What happens when $WE = 0$ ?

The circuit stores the last bit from **D**  
(same truth table  
as before!).

This circuit is  
called a  
**gated D latch**.


WE	D	R'	S'	Q	P
1	0	0	1	0	1
1	1	1	0	1	0
0	x	1	1	0	1
0	x	1	1	1	0

# This Design is Called a Gated D Latch

 

Symbolically, a **gated D latch** is drawn as shown here.

 Notice that **P** has been replaced by **Q'**, since they are always complements of one another.



University of Illinois at Urbana-Champaign  
Dept. of Electrical and Computer Engineering

# ECE 120: Introduction to Computing

---

## The Clock Abstraction

# Latches Can be Used Directly for Sequential Systems

---

Many high-speed designs are based on latches.

A set of latches serves as input to combinational logic.

The outputs are stored in latches.

And so forth. (Eventually making a loop.)



# Complemented Inputs are Usually “Free”

---

Now you can understand why **complemented inputs are usually “free”** (do not require inverters to generate).

If inputs come from latches, we can simply connect wires to the **Q** or to the **Q'** outputs.



# A Clock Signal is Idealized as a Square Wave


---

A **clock signal** is used to drive the **WE** inputs of the latches.

The clock is (ideally) a **square wave**.


So a **4 GHz** clock repeats:

 - **0.125 nanoseconds at 0V,**
- **0.125 nanoseconds at  $V_{dd}$ .**


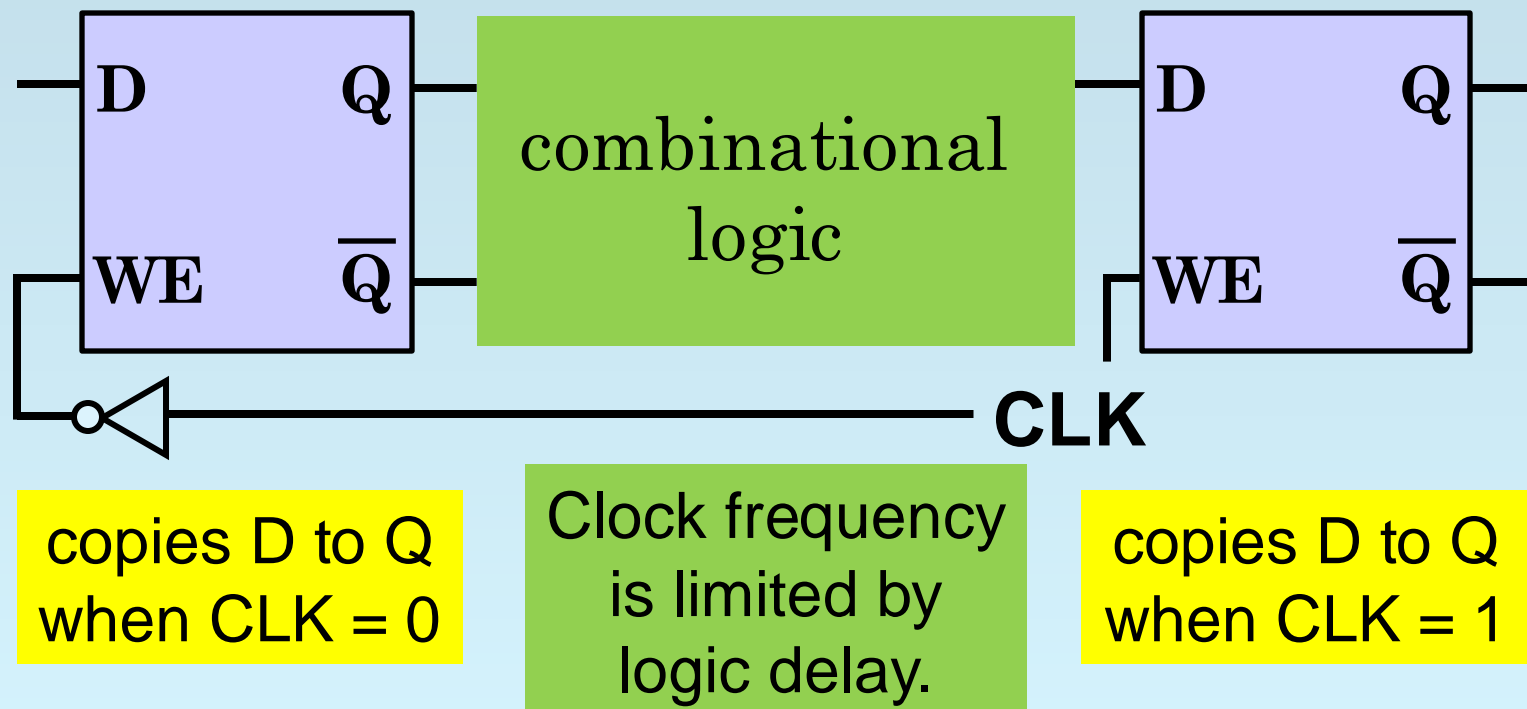
# Sets of Latches Alternate Write Enable Sense

Alternating sets of latches accept input in alternating clock phases (low and high).



# Reality is Substantially More Challenging

---

Ideally, the clock

- is a square wave, and
- edges arrive at all latches at the same time.

In the real world,

- there are **no square waves**, and
- “at the **same time**” is **not meaningful** (an effect of special relativity).

We will use a simpler abstraction.


And leave the problem of **clock skew** (timing of clock edges) to the circuit designers.



# Assume Flip-Flops and a Common Clock in Our Class

In particular, we combine consecutive sets of latches into “flip-flops” (as shown below), and only allow combinational logic between flip-flops.


no combinational logic here

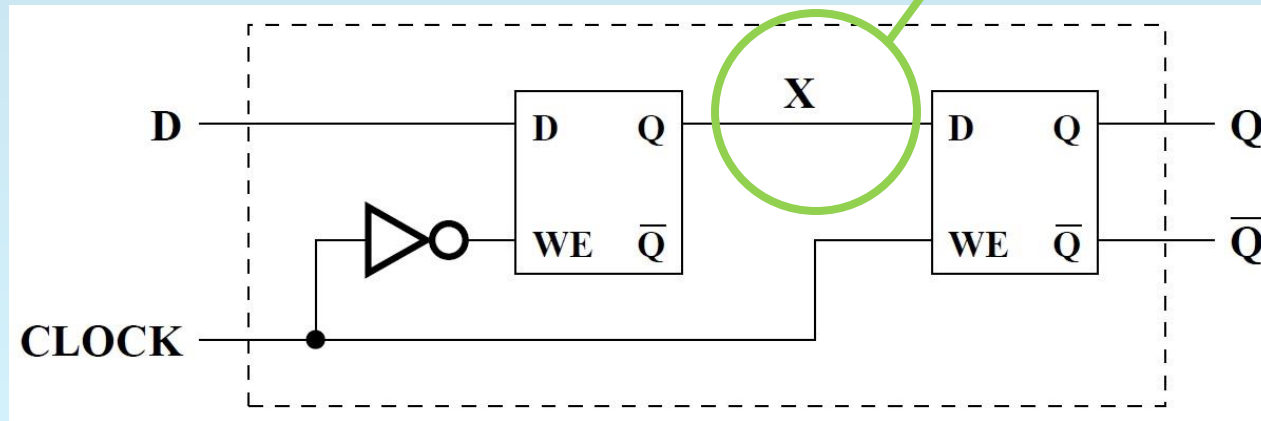

 
# Our Class Uses only One Type of Flip-Flop

Design below (symbol to right) shows

- a **master-slave implementation** (using two gated D latches) of
- a **positive-edge-triggered D flip-flop**.



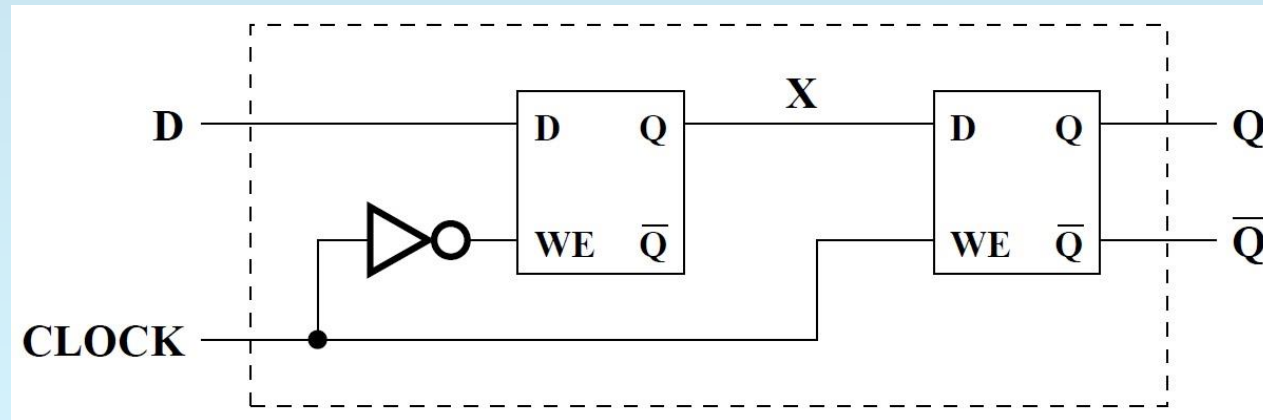Note the use of a triangle for the clock input.



# What Does the Name Mean?

---

A “**flip-flop**” stores one bit, and changes value **once each clock cycle**.

A “**D flip-flop**” accepts the bit to store **using a D(ata) input**.

“**Positive-edge-triggered**” means that the flip-flop’s value **changes on the rising edge** (low to high) of the clock signal.

# Our Simplifying Assumptions Imply Discrete Time

---

So what does our use of flip-flops  
and ignoring clock skew imply?

**Discrete time!**

Time is an integer.


Each clock cycle is one unit of time.

Flip-flops copy their **D** inputs to their **Q** outputs on the rising edge of the clock.

Between integer values of time,  
**we assume that nothing changes.**
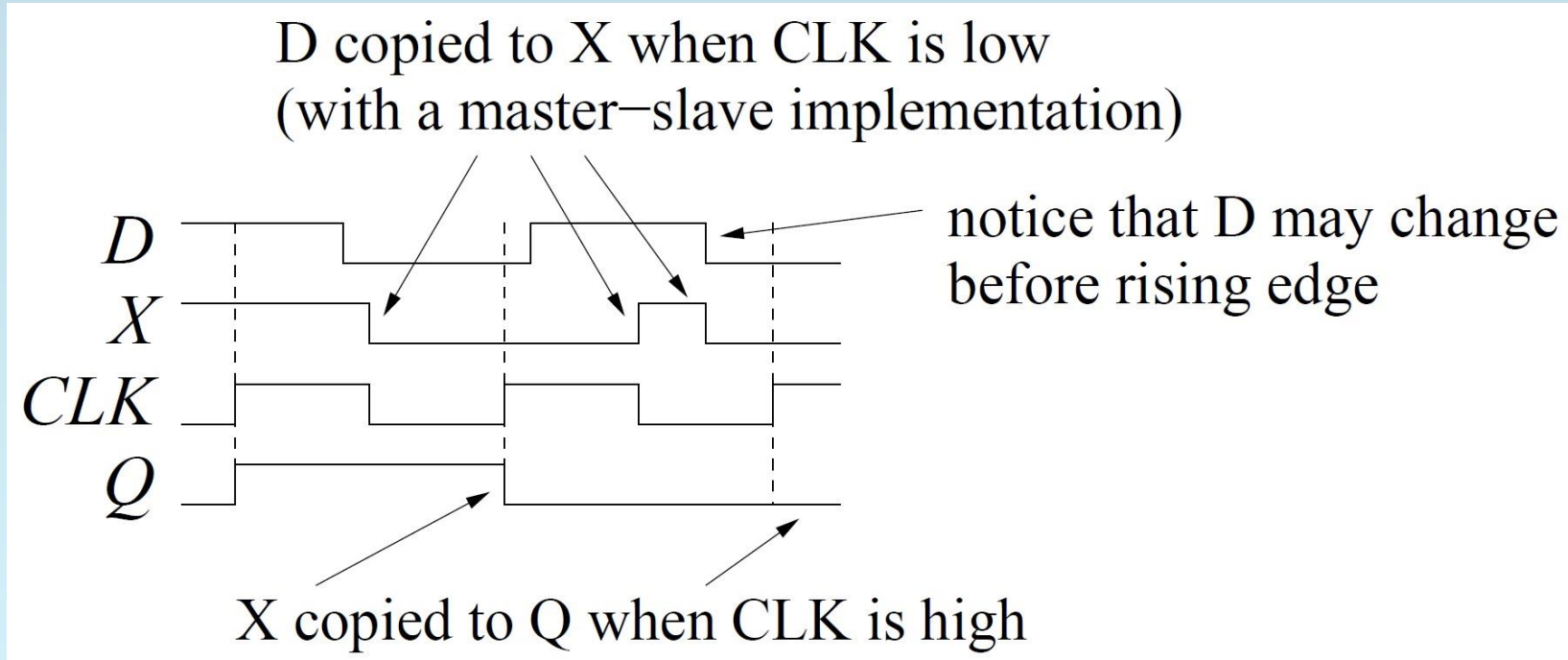
# Our Flip-Flop Stores a New Bit on Each Rising Clock Edge

Let's see how our flip-flop works internally.  
Remember that **X** is between the two latches.



# Our Flip-Flop Stores a New Bit on Each Rising Clock Edge

---

In our class, all of your designs for sequential systems will be **clocked synchronous sequential circuits**. These assume use of

- flip-flops (for us, positive-edge-triggered D flip-flops) and
- a common (synchronous) clock signal.

Components such as latches and flip-flops are examples of **sequential feedback circuits**. You should understand how they work, but we don't expect you to design any.